

[illegible][illegible]

RESISTANCE MEASUREMENT

Aim of experiment: To determine the resistance of a given wire using a meter bridge.

Apparatus: A meter bridge, Leclanche cell, key, resistance box, galvanometer, jockey, connecting wires, sand paper and wire of unknown resistance.

Theory: When the meter bridge is balanced, the resistance, X of the experimental wire is given by


$$X = R \frac{100 - l}{l}$$

where R = resistance introduced from the resistance box and l = length of wire between A and B (see fig.)

Exercise 1: Verify the laws of resistances in series and parallel

- Hints: (i) Connect resistance R_1 in gap (ii) and repeat the above experiment to determine R_1 .
 (ii) Remove R_1 and connect R_2 in gap (ii). Repeat the above experiment to determine R_2 .
 (iii) Connect R_1 and R_2 in series with each other, as shown fig. Connect this combination in gap (ii) and repeat the above experiment to determine the combined resistance R_s .
 (iv) Connect R_1 and R_2 in parallel with each other as shown in fig. connect this combination in gap (ii) and repeat the above experiment to determine the combined resistance R_p .
- $l_1 = 31.5$ cm $l_2 = 15.5$ cm

Teacher's Signature _____

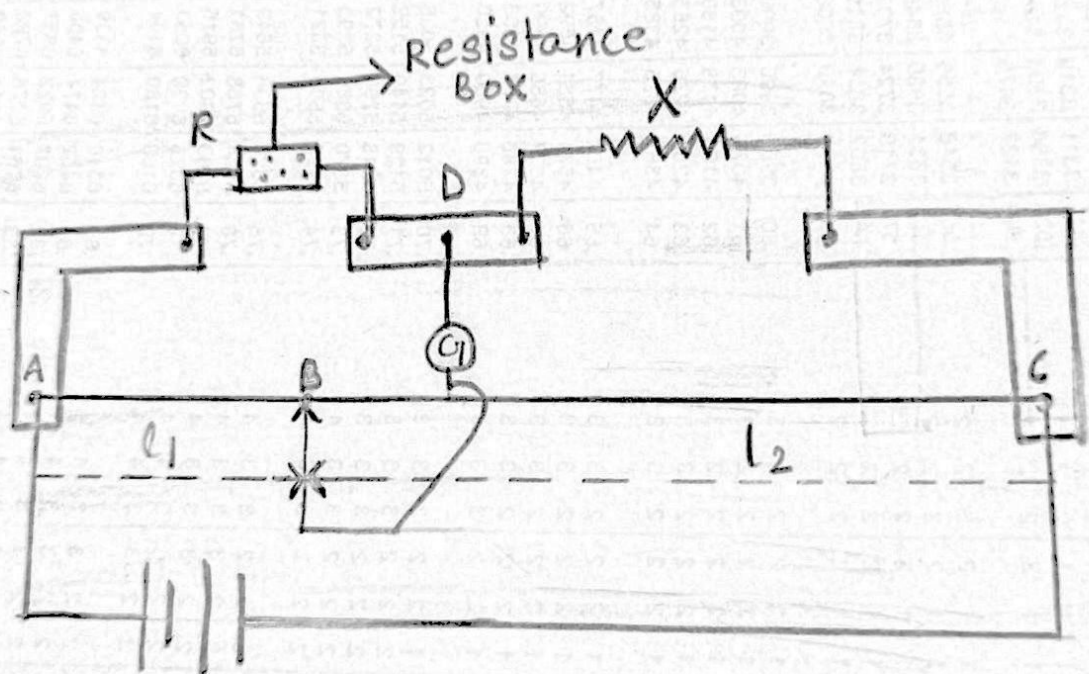

	Sl No.	R (ohm)	l ₁ (cm)		Mean l ₁ (cm)	$R = \frac{100 - l}{L}$
			(i)	(ii)		
X ₁	1.	0.2	11	11.2	11.1	1.6018
	2.	0.5	27.3	27.5	27.4	1.3450
	3.	0.7	26.5	26.7	26.6	1.9315
					Mean X ₁ =	1.6261 ohm
X ₂	1.	0.2	21.8	21.9	21.9	0.7132
	2.	0.5	39.2	39.3	39.3	0.7722
	3.	0.7	39.7	39.8	39.8	1.0587
					Mean X ₂ =	0.8480 ohm
R _s	1.	0.2	34.6	34.7	34.7	0.3763
	2.	0.5	19	19.1	19.1	2.1178
	3.	0.7	16.5	16.6	16.6	3.5168
					Mean R _s =	2.0036 ohm
R _p	1.	0.2	66.87	66.9	66.9	0.0989
	2.	0.5	42	42.1	42.1	0.6061
	3.	0.7	45.1	45.2	45.2	0.8486
					Mean R _p =	0.5178 ohm

Verification: From the above observation it can be observed that

(i) $R_s = X_1 + X_2 \Rightarrow (1.6261 + 0.8480) \Rightarrow 2.4741 \approx 2.0036$

This verify the law of resistance in series.

(ii) $R_p = \frac{X_1 X_2}{X_1 + X_2} \approx 0.557347237$

This verifies the law of resistance in parallel.

Exercise 2: Determine the specific resistance of the material of given wire

Hint : Resistance X of a wire is given by

$$X = \rho \frac{l}{a}$$

where, ρ = resistivity or specific resistance of the material of wire.

l = length of wire

a = area of cross-section of wire

r = radius of wire

$$\therefore \rho = \frac{Xa}{l} \quad \text{or} \quad \rho = \frac{X \cdot \pi r^2}{l}$$

- (i) Connect the given wire in gap(ii) and determine X as explained above.
- (ii) Cut the wire from the points where it emerges out of the terminals and find its length with the help of a meter rod.
- (iii) Find the diameter of the wire, with help of a screw gauge at three or four places. At each place the diameter should be determined in two mutually perpendicular directions.

(ii) Length of wire

$l =$ _____ cm
= _____ m

(iii) Diameter of the wire (with screw gauge)

Pitch of screw gauge (P) = 0.05 cm L.C. of
screw gauge = 0.001 cm

Teacher's Signature _____

No. of Obs.	I.C.S.R (I)	F.C.S.R (F)	No. of rotation(N)	C.S.R(I~F) X.L.C (cm)	P.S.R N x P (cm)	Total(d) PSR+CSR	$r = d/2$ SR (cm)	Mean (μ m)
1.	48	28	1	0.02	0.05	0.07	0.035	
2.	42	28	1	0.014	0.05	0.064	0.032	
3.	43	26	1	0.015	0.05	0.065	0.0326	0.034
4.	47	26	1	0.019	0.05	0.069	0.0345	
5.	3	26	1	0.025	0.05	0.075	0.0375	

Radius of the wire $r = \frac{D}{2} = 0.034 \text{ cm}$

Calculations :

$$P_1 = \frac{X_2 \pi r^2}{l_1} = \frac{1.6261 \times 3.14 \times (0.0343)^2}{31.5}$$

$$P_1 = 1.907 \times 10^{-4} \text{ ohm meter.}$$

$$P_2 = \frac{X_2 \pi r^2}{l_2} = \frac{0.8460 \times 3.14 \times (0.0343)^2}{15.5}$$

$$P_2 = 2.021 \times 10^{-4} \text{ ohm meter.}$$

$$\sigma_1 = \frac{1}{P_1} = 0.5243 \times 10^4$$

$$\sigma_2 = \frac{1}{P_2} = 0.4948 \times 10^4$$