 


II PRE LAB

Objective 1

a State Diagram:




State Table:

Present State		Next State		Flip Flop inputs		
A	B	A	B	D_A	D_B	D_C
0	0	0	1	0	1	
0	1	1	0	1	0	
1	0	1	1	1	1	
1	1	0	0	0	0	

$$D_A = A'B + AB'$$

$$= A \oplus B$$

$$D_B = B'$$

 

```


b) module dff (
    input D, clk,
    output Q
);
    reg Q
    always @ (posedge clk)
        Q <= D
    end module

module Counter (
    input d, clk, reset,
    output Q0, Q1
);
    dff d1((Q0 ^ Q1), clk, reset, Q0)
    dff d2(Q1, clk, reset, Q1)
end module.

```

Objective 2

a) State Diagram.

 

State Table.

Present State		Next State		Flip-Flop input			
A	B	A	B	J_A	K_A	J_B	K_B
0	0	1	1	1	X	1	X
0	1	0	0	0	X	X	1
1	0	0	1	X	1	1	X
1	1	1	0	X	0	X	1

$J_A \backslash B$	0	1
0	1	0
1	X	X


B'

$K_A \backslash B$	0	1
0	X	X
1	1	

B'

$$J_A = K_A = B'$$

$$J_B = K_B = 1$$

 

b) module jkff(
input j, k, clk, clear;
output Q;
);
reg Q;
always @(posedge (clk))
begin
if (~clear) begin
Q = 1'b0;
end
else
begin
case ({j, k})
2'b00: Q <= Q;
2'b01: Q <= 0;
2'b10: Q <= 1;
2'b11: Q <= ~Q;
endcase
end
end

end case

end

end

end module

module counter C

input J, K, clk, clear;

output Q0, Q1;

);

~~two~~ jkff A(1,1, clk, clear, Q0);


jkff B(Q0, ~Q0, clk, clear, Q1);

end module

Page:



Objective 3

a) State Diagram

 


State diagram.

Present State			Next State			Flip Flop Inputs		
A	B	C	A	B	C	T _A	T _B	T _C
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

  

$$T_A = BC, T_B = C, T_C = 1$$

 

b) module tff(
input T, clk, clear;
output Q;
);
reg Q;
always @ (posedge (clk))
begin
if (~clear)
begin
Q = 1'b0;
end
else
begin
Q = T ^ Q;
end
end
end module.


```

module counter (
    input T, clk, clear;
    output Q0, Q1, Q2
);
    tff ((Q2 & Q1), clk, clear);
    tff (Q2, clk, clear);
    tff (1, clk, clear);
endmodule

```

III LAB

Components Required.

S.No	Name of the Component	Specification	Quantity
1	D-Flip Flop	IC-7474	1
2	J-K Flip-Flop	IC-7476	2
3	XOR gates	IC-7486	1
4	AND gates	IC-7408	1
5	Connecting Wires	23 SW G	As per required

Conclusion

Obj 1 - It can be concluded that 2 D-Flip Flop are used to Design 2 bit Synchronous up counter

Obj 2 - It can be concluded that 2 JK Flip Flops are used to Design 2 bit Synchronous up/down counter.

Obj 3 - It can be concluded that 3 T Flip Flops are used to Design 3 bit Synchronous Up Counter.


IV POST LAB

$$\begin{array}{r} 1 \quad 1001100111 \\ \quad \quad \quad +1 \\ \hline 1001101000 \end{array}$$

Page



Ans - 4 Flip-Flops will be complemented.

2 State diagram

 

State table:

Present State			Next State			Flip Flop inputs		
A	B	C	A	B	C	D _A	D _B	D _C
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	1	0	0	1	0	0
0	1	1	x	x	x	x	x	x
1	0	0	1	1	0	1	1	0
1	0	1	x	x	x	x	x	x
1	1	0	0	0	0	0	0	0
1	1	1	x	x	x	x	x	x

  

D_c

	00	01	11	10
0	1		X	
1		X	X	

$$Dc = A'Bc'$$

